



## DAY-1

### #100DAYSOFRTL

**Aim:-** Basic Logic gates implementation using NAND(Universal gate)


#### RTL CODE:-

```
///Date:-01/01/2024
module Nand_gate(
input a,b, output y_not,y_and,y_or,y_nor,y_xor,
y_xnor);
wire w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12,w13;
○ nand g1(y_not,a,a); ///NOT GATE
○ nand g2(w1,a,b);
○ nand g3(y_and,w1,w1);///AND GATE
○ nand g4(w2,a,a);
○ nand g5(w3,b,b);
○ nand g6(y_or,w1,w2); ///OR GATE
○ nand g7(w4,a,a);
○ nand g8(w5,b,b);
○ nand g9(w6,w4,w5);
○ nand g10(y_nor,w6,w6);///NOR GATE
○ nand g11(w7,a,b);
○ nand g12(w8,a,w7);
○ nand g13(w9,b,w7);
○ nand g14(y_xor,w8,w9);///XOR GATE
○ nand g15(w10,a,b);
○ nand g16(w11,a,w10);
○ nand g17(w12,b,w10);
○ nand g18(w13,w11,w12);
○ nand g19(y_xnor,w13,w13);///xnor GATE
endmodule
```

#### OUTPUT:-

```
a=0,b=0,y_not=1,y_and=0,y_or=0,y_nor=1,y_xor=0,y_xnor=1
a=0,b=1,y_not=1,y_and=0,y_or=0,y_nor=0,y_xor=1,y_xnor=0
a=1,b=0,y_not=0,y_and=0,y_or=1,y_nor=0,y_xor=1,y_xnor=0
a=1,b=1,y_not=0,y_and=1,y_or=1,y_nor=0,y_xor=0,y_xnor=1
```

## WAVEFORMS:-

 

### SCHEMATIC:-

