



DAY-9

#100DAYSOFRTL

Aim:- Implementation of 4-Bit Ripple Carry Adder using Full Adder.

Ripple carry adder is Obtained by instantiating 4 Full adders.

RTL CODE:-

```
1  |  ///DATE:-09/01/2024
2  |  ///4-BIT RIPPLE CARRY ADDER
3  |  module FA(input A,B,Cin,
4  |  output Sum,Carry);
5  |  assign Sum=A^B^Cin;
6  |  assign Carry=A&B|B&Cin|Cin&A;
7  |  endmodule
8  |
9  |  module Ripplecarry_Adder(input [3:0] A,
10 |  input [3:0] B,
11 |  input Cin, output [4:0] Sum);
12 |  wire w1,w2,w3;
13 |  FA M1(.A(A[0]),.B(B[0]),.Cin(Cin),.Carry(w1),.Sum(Sum[0]));
14 |  FA M2(.A(A[1]),.B(B[1]),.Cin(w1),.Carry(w2),.Sum(Sum[1]));
15 |  FA M3(.A(A[2]),.B(B[2]),.Cin(w2),.Carry(w3),.Sum(Sum[2]));
16 |  FA M4(.A(A[3]),.B(B[3]),.Cin(w3),.Carry(Sum[4]),.Sum(Sum[3]));
17 |  endmodule
```


TESTBENCH:-

```
1 module Ripplecarry_tb();
2   reg [3:0]A,B;
3   reg Cin;
4   wire [4:0] Sum;
5   Ripplecarry_Adder dut (.A(A), .B(B), .Cin(Cin), .Sum(Sum));
6 initial begin
7   A=4'b0000; B=4'b0000; Cin=0;
8   #10;
9   $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
10  A=4'b0001; B=4'b1000; Cin=1;
11  #10;
12  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
13  A=4'b0010; B=4'b0010; Cin=1;
14  #10;
15  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
16  A=4'b0111; B=4'b0111; Cin=0;
17  #10;
18  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
19  A=4'b0111; B=4'b1000; Cin=1;
20  #10;
21  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
22  A=4'b0001; B=4'b1000; Cin=0;
23  #10;
24  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
25  A=4'b0011; B=4'b1100; Cin=1;
26  #10;
27  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
28  A=4'b1111; B=4'b1111; Cin=0;
29  #10;
30  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
31  A=4'b0111; B=4'b0011; Cin=1;
32  #10;
33  $display("A=%d,B=%d,Cin=%b,Sum=%d",A,B,Cin,Sum);
34  $finish();
35 end
36 endmodule
```

OUTPUT:-

```
A= 0,B= 0,Cin=0,Sum= 0
A= 1,B= 8,Cin=1,Sum=10
A= 2,B= 2,Cin=1,Sum= 5
A= 7,B= 7,Cin=0,Sum=14
A= 7,B= 8,Cin=1,Sum=16
A= 1,B= 8,Cin=0,Sum= 9
A= 3,B=12,Cin=1,Sum=16
A=15,B=15,Cin=0,Sum=30
A= 7,B= 3,Cin=1,Sum=11
```

SCHEMATIC:-

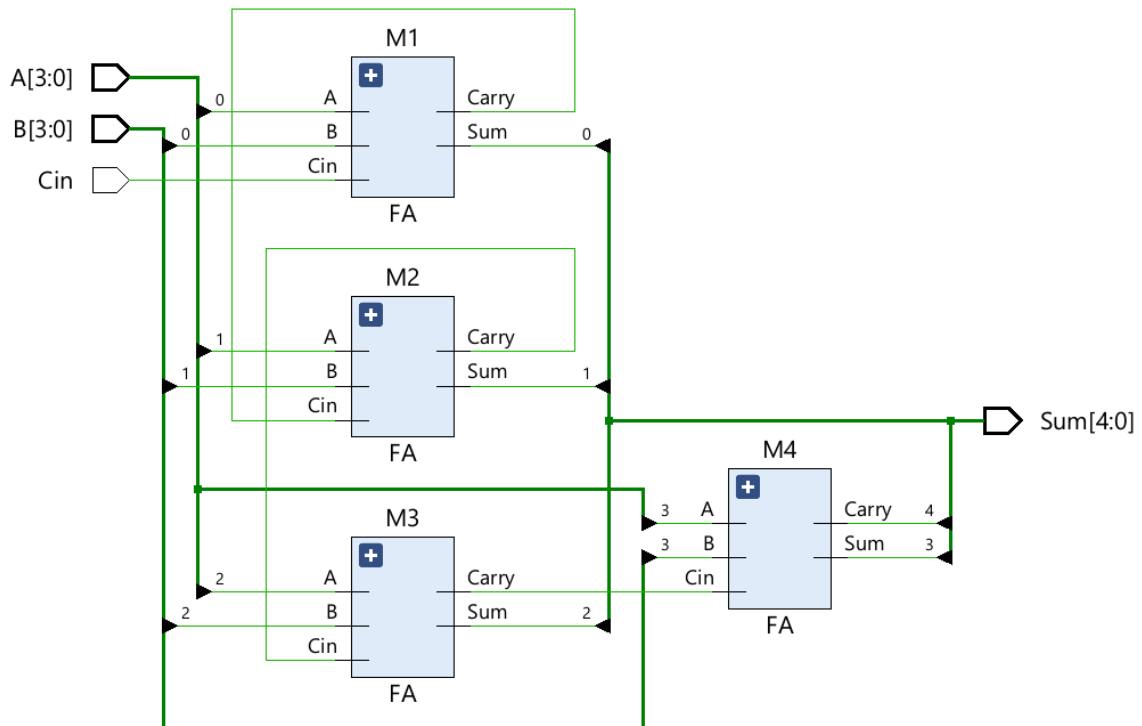

WAVEFORMS:-

