



DAY-76

#100DAYSOFRTL

Aim:- Implementation of **T FLIPFLOP** to **JK FLIPFLOP**.

RTL CODE:-

```
1  ///DATE:-16/03/2024
2  ///DAY-76
3  ///Implementation of T FF to JK FF
4  module Day_76(input clk,rst,J,K,output q,qbar);
5      wire w1,w2,w3;
6      and g1(w1,J,qbar);
7      and g2(w2,K,q);
8      or g3(w3,w1,w2);
9      Tff TFF(clk,rst,w3,q,qbar);
10 endmodule
11
12 ///T-Flipflop
13 module Tff(input clk,rst,T,
14 output reg q, output qbar);
15 always @(posedge clk) begin
16     if(rst) begin
17         q<=0;
18     end
19     else begin
20         case(T)
21             1'b0:{q}={q};
22             1'b1:{q}={~q};
23         endcase
24     end
25 end
26 assign qbar=~q;
27 endmodule
~~
```

OUTPUT:-

```
J=0,K=0,q=0,qbar=1
J=0,K=1,q=0,qbar=1
J=1,K=0,q=1,qbar=0
J=1,K=1,q=0,qbar=1
```


TESTBENCH:-

```

1 module Day_76_tb();
2   reg clk,rst,J,K;
3   wire q,qbar;
4   Day_76 uut(clk,rst,J,K,q,qbar);
5   always #5 clk=~clk;
6   initial
7   clk=0;
8   initial begin
9     rst=1; #10;
10    rst=0;
11    J=0; K=0; #10;
12    $display("J=%b,K=%b,q=%b,qbar=%b",J,K,q,qbar);
13    J=0; K=1; #10;
14    $display("J=%b,K=%b,q=%b,qbar=%b",J,K,q,qbar);
15    J=1; K=0; #10;
16    $display("J=%b,K=%b,q=%b,qbar=%b",J,K,q,qbar);
17    J=1; K=1; #10;
18    $display("J=%b,K=%b,q=%b,qbar=%b",J,K,q,qbar);
19    $finish();
20  end
21 endmodule

```

WAVEFORMS:-

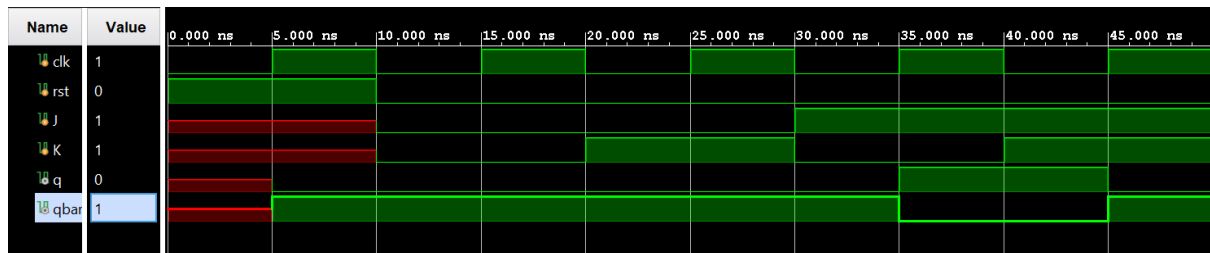

SCHEMATIC:-

