


DAY-69 #100DAYSOFRTL

Aim:- Implementation of T F/F TO D F/F using Verilog.

RTL CODE:-

```
///DATE:-09/03/2024
   !///DAY-69
   \c ////Implementation of T f/f to D f/f
   module Day_69(input clk,rst,D,
   output q,qbar);
   wire w1;
O |xor g1(w1,D,q);
   Tff tflipflop(clk,rst,w1,q,qbar);
   endmodule
   module Tff(input clk,rst,T,
   output reg q, output qbar);
O always @(posedge clk) begin
O if(rst) begin
O q<=0;
   end!
   else begin
O case(T)
1'b0:{q}={q};
O |1'b1:{q}={~q};
   endcase
   end
   end!
O |assign qbar=~q;
   endmodule
```

WAVEFORMS:-

 


TESTBENCH:-

```
module Day_69_tb();
   reg clk,rst,D;
   wire q,qbar;
   Day_69 uut(clk,rst,D,q,qbar);
O always #5 clk=~clk;
O initial clk=0;
  initial begin
O rst=1; #10;
O |rst=0;
O |D=0; #10;
$\display("D=%b,q=%b,qbar=%b",D,q,qbar);
O D=1; #20;
$\display("D=%b,q=%b,qbar=%b",D,q,qbar);
O |D=0; #10;
Sdisplay("D=%b,q=%b,qbar=%b",D,q,qbar);
O D=1; #20;
$\$\display("D=\%b,q=\%b,q\bar=\%b",D,q,q\bar);

$finish();
   end
   endmodule
```

SCHEMATIC:-

 

OUTPUT:-

```
D=0,q=0,qbar=1
D=1,q=1,qbar=0
D=0,q=0,qbar=1
D=1,q=1,qbar=0
```

