



DAY-18

#100DAYSOFRTL

Aim:- Implementation of 8-BIT Subtractor.

RTL CODE:-

```

    ///DATE:-18/01/2024
    ///Implementation of 8-BIT Subtractor
    module Subtractor(input [7:0] A,B,
    output reg [7:0] sub);
    ○ reg [7:0] Temp_sub;
    ○ always@(*) begin
    ○ Temp_sub=(~B)+1'b1;///2'S COMPLEMENT SUBTRACTION;
    sub=Temp_sub+A;
    end
    endmodule

```

TESTBENCH:-

```


    module Sub_tb();
    reg [7:0] A,B;
    wire [7:0] sub;
    Subtractor uut(A,B,sub);
    initial begin
    ○ for(integer i=0; i<10; i=i+1)
    begin
    ○ A=$random();
    ○ B=$random();
    ○ #10;
    ○ $display("A=%d,B=%d,sub=%d",A,B,sub);
    ○ #10;
    end
    end
    initial begin
    ○ #300;
    ○ →$finish();
    end
    endmodule

```


OUTPUT:-

```
A= 36,B=129,sub=163
A= 9,B= 99,sub=166
A= 13,B=141,sub=128
A=101,B= 18,sub= 83
A= 1,BB= 13,sub=244
A=118,B= 61,sub= 57
A=237,B=140,sub= 97
A=249,B=198,sub= 51
A=197,B=170,sub= 27
A=229,B=119,sub=110
```

SCHEMATIC:-

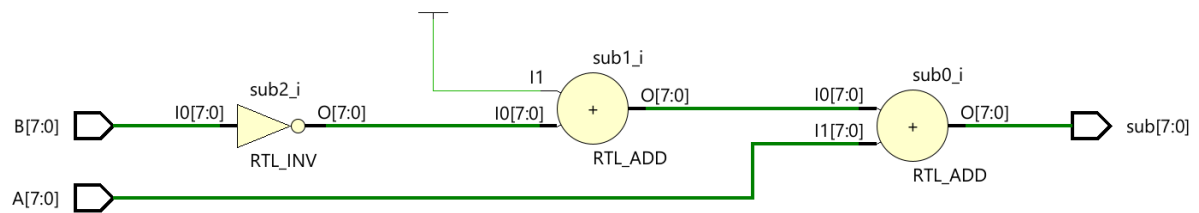

WAVEFORMS:-

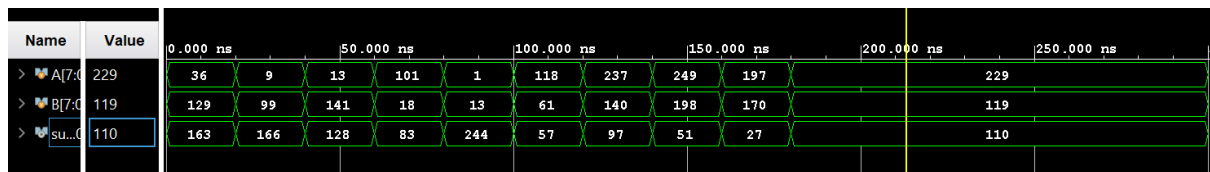

=====