



DAY-2

#100DAYSOFRTL

Aim:- Basic Logic gates implementation using NOR GATE(Universal gate)

 
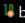
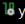
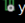
 
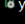

 
RTL CODE:-

```
1 //DATE:-02/01/2024
2 //Gate level Modelling
3 module Nor_Gate(input a,b,output y_not,
4   y_or,y_and,y_nand,y_xor,y_xnor);//Port declaration
5   wire [12:0] W; //wire declaration
6   nor g1(y_not,a,a);//NOT GATE
7   nor g2(W[0],a,b);
8   nor g3(y_or,W[0],W[0]);//OR GATE
9   nor g4(W[1],a,a);
10  nor g5(W[2],b,b);
11  nor g6(y_and,W[1],W[2]);//AND GATE
12  nor g7(W[3],a,a);
13  nor g8(W[4],b,b);
14  nor g9(W[5],W[3],W[4]);
15  nor g10(y_nand,W[5],W[5]);//NAND GATE
16  nor g11(W[6],a,b);
17  nor g12(W[7],a,W[6]);
18  nor g13(W[8],b,W[6]);
19  nor g14(y_xnor,W[7],W[8]);//XNOR GATE
20  nor g15(W[9],a,b);
21  nor g16(W[10],a,W[9]);
22  nor g17(W[11],b,W[9]);
23  nor g18(W[12],W[10],W[11]);
24  nor g19(y_xor,W[12],W[12]); //XOR GATE
25 endmodule
```

OUTPUT:-

```
a=0,b=0,y_not=1,y_and=0,y_or=0,y_nand=1,y_xor=0,y_xnor=1
a=0,b=1,y_not=1,y_and=0,y_or=1,y_nand=1,y_xor=1,y_xnor=0
a=1,b=0,y_not=0,y_and=0,y_or=1,y_nand=1,y_xor=1,y_xnor=0
a=1,b=1,y_not=0,y_and=1,y_or=1,y_nand=0,y_xor=0,y_xnor=1
```

TESTBENCH:-

Name	Value	0.000 ns	5.000 ns	10.000 ns	15.000 ns	20.000 ns	25.000 ns	30.000 ns	35.000 ns	40.000 ns	45.000 ns
 a	1										
 b	1										
 y_no	0										
 y_an	1										
 y_or	1										
 y_and	0										
 y_xor	0										
 y_xnv	1										



=====