




## DAY-16

### #100DAYSOFRTL

**Aim:-** Implementation of 2X2 BIT MULTIPLIER Using Verilog.

#### BLOCK DIAGRAM:-

 

Schematic of 2x2 Bit Multiplier Using Single Bit Adder

#### RTL CODE:-

```
//////DATE:-16/01/2024
//////Implementation of Two Bit Multiplier(2X2)
module HalfAdder(input A,B,
output Sum,Carry);
  assign Sum=A^B;
  assign Carry=A&B;
endmodule

module Two_BitMul(input [1:0]A,B,
output [3:0] P);
  wire [3:0]W;
  and g1(P[0],A[0],B[0]);
  and g2(W[0],A[0],B[1]);
  and g3(W[1],A[1],B[0]);
  and g4(W[2],A[1],B[1]);
  HalfAdder M0(.A(W[1]),.B(W[0]),.Sum(P[1]),.Carry(W[3]));
  HalfAdder M1(.A(W[2]),.B(W[3]),.Sum(P[2]),.Carry(P[3]));
endmodule
```


## TESTBENCH:-

```
module Two_BitMul_tb();  
  reg [1:0] A,B;  
  wire [3:0] P;  
  Two_BitMul uut(.A(A),.B(B),.P(P));  
  initial begin  
    ○ for(integer i=0; i<10; i=i+1) begin  
    ○ A=$random();  
    ○ B=$random();  
    ○ #10;  
    ○ $display("A=%d,B=%d,P=%d",A,B,P);  
    ○ #10;  
    end  
  end  
  initial begin  
    ○ #200;  
    ○ → $finish();  
  end  
endmodule
```

## OUTPUT:-

```
A=0,B=1,P= 0  
A=1,B=3,P= 3  
A=1,B=1,P= 1  
A=1,B=2,P= 2  
A=1,B=1,P= 1  
A=2,B=1,P= 2  
A=1,B=0,P= 0  
A=1,B=2,P= 2  
A=1,B=2,P= 2  
A=1,B=3,P= 3
```

## SCHEMATIC:-

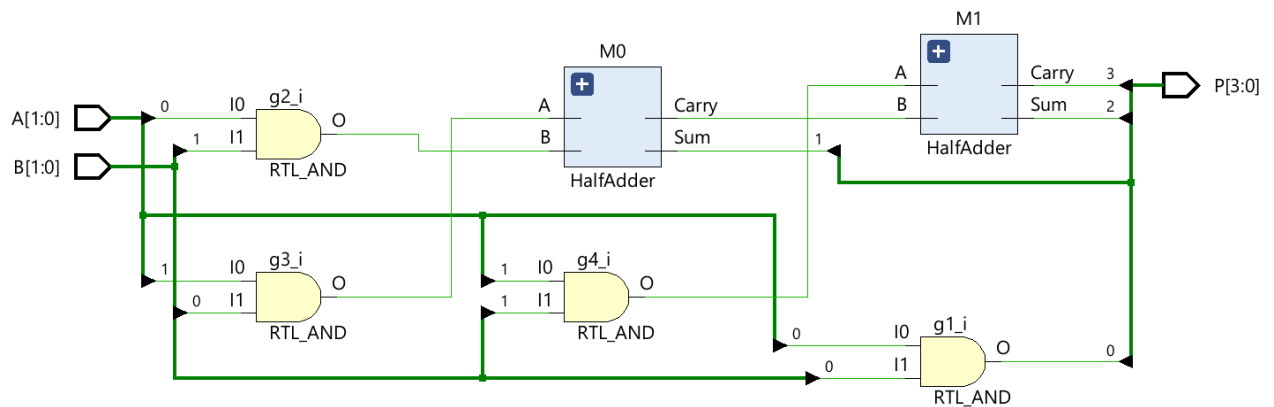

## WAVEFORMS:-

