



DAY-97

#100DAYSOFRTL


Aim:- Implementation of Clock Divider by 6(F/6).

RTL CODE:-

```
//////DATE:-06/04/2024
//////DAY-97
////Implementation of Frequency Divider by 5
module Day_97(input clk,rst,en, output div6);
  wire w1;
  reg [2:0] cnt;
  always@(posedge clk) begin
    if(rst)
      cnt<=3'd0;
    else if(en) begin
      if(cnt==3'd5)
        cnt<=0;
      else
        cnt<=cnt+1;
    end
  end
  Dff dflop(clk,rst,cnt[2],w1);
  or g1(div6,w1,cnt[2]);
endmodule

module Dff(input clk,rst, D, output reg q);
  always @(posedge clk) begin
    if(rst)
      q<=0;
    else begin
      case (D)
        1'b0:q<=0;
        1'b1:q<=1;
      endcase
    end
  end
endmodule
```

WAVEFORMS:-

 

TESTBENCH:-

```
module Day_97_tb();  
    reg clk,rst,en;  
    wire div6;  
    Day_97 uut (clk,rst,en,div6);  
    ○ always #5 clk=~clk;  
    ○ initial clk=0;  
    initial begin  
    ○ rst=1; #10;  
    ○ rst=0;  
    ○ en=1;  
    end  
endmodule
```

SCHEMATIC:-

