




**DAY-17**

**#100DAYSOFRTL**

**Aim:-** Implementation of 4X4 BIT ARRAY MULTIPLIER  
IN GATE LEVEL MODELLING

**BLOCK DIAGRAM:-**

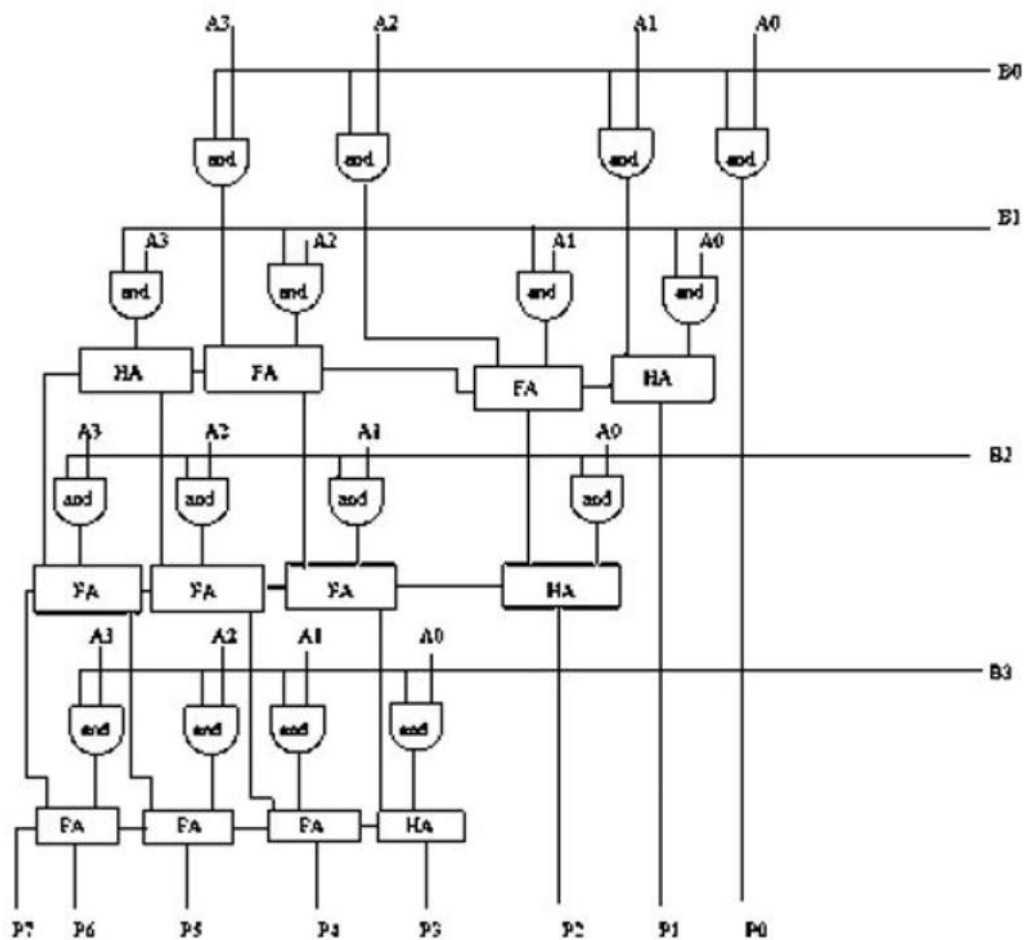

# RTL CODE:-

```
//////DATE:-17/01/2024
//////Implementation of 4X4 BIT Multiplier
module HalfADDER(input A,B,
output S,C);
○ assign S=A^B;
○ assign C=A&B;
endmodule

module Fa(input A,B,Cin,
output Sum,Cout);
○ assign Sum=A^B^Cin;
○ assign Cout=A&B|B&Cin|Cin&A;
endmodule

module Mul(input [3:0] A,B,
output [7:0] P);
wire [15:0]W;
wire [11:0]I;
wire [5:0] F;
○ and g1(P[0],A[0],B[0]);
○ and g2(W[0],A[1],B[0]);
○ and g3(W[1],A[2],B[0]);
○ and g4(W[2],A[3],B[0]);

○ and g5(W[3],A[0],B[1]);
○ and g6(W[4],A[1],B[1]);
○ and g7(W[5],A[2],B[1]);
○ and g8(W[6],A[3],B[1]);

○ and g9(W[7],A[0],B[2]);
○ and g10(W[8],A[1],B[2]);
○ and g11(W[9],A[2],B[2]);

○ and g12(W[10],A[3],B[2]);

○ and g13(W[11],A[0],B[3]);
○ and g14(W[12],A[1],B[3]);
○ and g15(W[13],A[2],B[3]);
○ and g16(W[14],A[3],B[3]);

HalfADDER K1(W[0],W[3],P[1],I[0]);
Fa K2(W[1],W[4],I[0],F[0],I[1]);
Fa K3(W[2],W[5],I[1],F[1],I[2]);
HalfADDER K4(W[6],I[2],F[2],I[3]);

HalfADDER K5(W[7],F[0],P[2],I[4]);
Fa K6(W[8],F[1],I[4],F[3],I[5]);
Fa K7(W[9],F[2],I[5],F[4],I[6]);
Fa K8(W[10],I[3],I[6],F[5],I[7]);

HalfADDER K9(W[11],F[3],P[3],I[8]);
Fa K10(W[12],F[4],I[8],P[4],I[9]);
Fa K11(W[13],F[5],I[9],P[5],I[10]);
Fa K12(W[14],I[7],I[10],P[6],P[7]);

endmodule
```

## TESTBENCH:-

```
module Mul_tb();  
    reg [3:0] A,B;  
    wire [7:0] P;  
    Mul uut(A,B,P);  
    initial begin  
        for(integer i=0; i<16; i=i+1) begin  
            A=$random();  
            B=$random();  
            #10;  
            $display("A=%d,B=%d,P=%d",A,B,P);  
            #10;  
        end  
    end  
    initial begin  
        #300;  
        →$finish();  
    end  
endmodule
```

## OUTPUT:-

```
A= 4,B= 1,P= 4  
A= 9,B= 3,P= 27  
A=13,B=13,P=169  
A= 5,B= 2,P= 10  
A= 1,B=13,P= 13  
A= 6,B=13,P= 78  
A=13,B=12,P=156  
A= 9,B= 6,P= 54  
A= 5,B=10,P= 50  
A= 5,B= 7,P= 35  
A= 2,B=15,P= 30  
A= 2,B=14,P= 28  
A= 8,B= 5,P= 40  
A=12,B=13,P=156  
A=13,B= 5,P= 65
```

## WAVEFORMS:-

Name	Value	0.000 ns50.000 ns100.000 ns150.000 ns200.000 ns250.000 ns300														
> A[3:0]	13	4	9	13	5	1	6	13	9	5	2	8	12	13		
> B[3:0]	5	1	3	13	2	13	12	6	10	7	15	14	5	13	5	
> P[7:0]	65	4	27	169	10	13	78	156	54	50	35	30	28	40	156	65

## SCHEMATIC:-

