

# DAY-28 #100DAYSOFRTL

**Aim:-** Implementation of 1:8 Demultiplexer Using Verilog.

## **RTL CODE:-**

```
:///DATE:-28/01/2024
   ////Implementation of 1:8 Demux using Behavioral modelling
O module Demux_1x8(input i,
input [2:0] Sel, output reg [7:0]y);
O always @(*) begin
O case (Sel)
\bigcirc \3'b000:y={7'b0,i};
○ 3'b001:y={6'b0,i,1'b0};
O '3'b010:y={5'b0,i,2'b0};
O |3'b011:y={4'b0,i,3'b0};
O \\3'b100:y={3'b0,i,4'b0};
O 3'b101:y={2'b0,i,5'b0};
   3'b110: y={1'b0, i, 6'b0};
   3'b111:y={i,7'b0};
   endcase
   end
   |endmodule
```

#### **OUTPUT:-**

```
i=0, Sel=1, y= 0
i=1, Sel=3, y= 8
i=1, Sel=5, y= 32
i=1, Sel=2, y= 4
i=1, Sel=5, y= 32
i=0, Sel=5, y= 0
i=1, Sel=4, y= 16
i=1, Sel=6, y= 64
i=1, Sel=2, y= 4
i=1, Sel=7, y=128
i=0, Sel=7, y= 0
```


## **TESTBENCH:-**

```
module Demux1x8_tb();
   reg i;
   reg [2:0] Sel;
   wire [7:0] y;
   Demux_1x8 uut(i,Sel,y);
   initial begin
\bigcirc |for(int k=0; k<15; k=k+1) begin
O i=$random();
O |Sel=$random();
O #10;
$\display("i=%d,Sel=%d,y=%d", i,Sel,y);
O #10;
   'end
   end
   initial begin
0 #300;
⇒$finish();
   end
   endmodule
```

#### **WAVEFORMS:-**

li 1	
> ♥ Sel 5 3 5 2 5 4	6
> ® y[7:0 32 8 32 4 32 0 16	64

## **SCHEMATIC:-**

 



\_\_\_\_\_