



DAY-75

#100DAYSOFRTL

Aim:- Implementation of **16-BIT DEPTH SYNCHRONOUS FIFO**(First-in First-out).


RTL CODE:-

```
//////DATE:-15/03/2024
//////DAY-75
//////Implementation of 16 BIT FIFO
module Day_75(input clk,rst,wr,rd,
input [7:0] data_in, output empty,full,
output reg [7:0] data_out);
  reg [3:0] wptr,rptr=0;
  reg [4:0] cnt=0;
  reg [7:0] mem[15:0] ;
  always @(posedge clk) begin
    if(rst==1'b1)
      begin
        wptr<=0;
        rptr<=0;
        cnt<=0;
      end
    else if(wr && (!full))
      begin
        mem[wptr]<=data_in;
        wptr<=wptr+1;
        cnt<=cnt+1;
      end
    else if(rd && (!empty))
      begin
        data_out<=mem[rptr];
        rptr<=rptr+1;
        cnt<=cnt-1;
      end
    end
  end
  assign empty=(cnt==0)?1'b1:1'b0;
  assign full=(cnt==16)?1'b1:1'b0;
endmodule
```

TESTBENCH:-

```
module Day_75_tb();
    reg clk,rst,wr,rd;
    reg [7:0] data_in;
    wire empty,full;
    wire [7:0] data_out;
    Day_75 uut (clk,rst,wr,rd,data_in,empty,full,data_out);
    always #5 clk=~clk;
    initial clk=0;
    initial begin
        rst=1;
        #10;
        rst=0;
        wr=1; /////Testing for write data
        data_in=8'd123;
        #10;
        wr=1; /////Testing for write data
        data_in=8'd12;
        #10;
        wr=1; /////Testing for write data
        data_in=8'd97;
        #10;
        rd=1;
        //rd=1;
        #300;
        $finish();
    end
endmodule
```

WAVEFORMS:-

 

SCHEMATIC:-

