




## DAY-15

### #100DAYSOFRTL

**Aim:-** Implementation of Binary Adder/Subtractor Circuit with control input.

**Block Diagram:-**

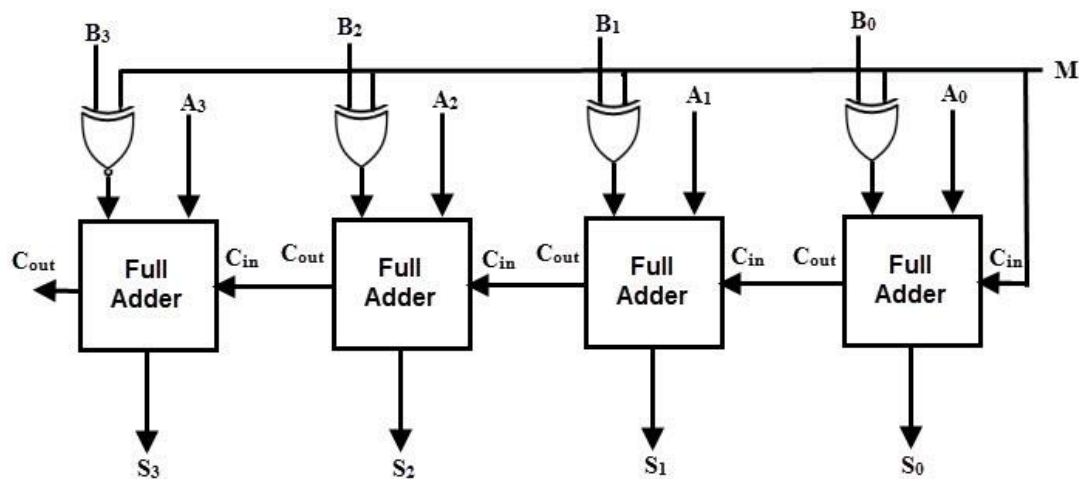

**RTL CODE:-**

```
//////DATE:-15/01/2024
//////4-BIT BINARY ADDER AND SUBTRACTOR WITH CONTROL INPUT
module FUAdder(input A,B,Cin,
output Sum,Cout);
○ assign Sum=A^B^Cin;
○ assign Cout=A&B|B&Cin|Cin&A;
endmodule

module Adder_Subtractor(input [3:0]A,B,
input Cin, output [3:0] Sum,
output Cout );
wire [2:0]C;
wire [3:0] W;
○ xor g1(W[0],B[0],Cin);///Cin=0=ADDER
○ xor g2(W[1],B[1],Cin);///Cin=1=Subtractor
○ xor g3(W[2],B[2],Cin);///Exceeds 15 Subtraction takes 2's complement
○ xor g4(W[3],B[3],Cin);
FUAdder F1(.A(A[0]),.B(W[0]),.Cin(Cin),.Sum(Sum[0]),.Cout(C[0]));
FUAdder F2(.A(A[1]),.B(W[1]),.Cin(C[0]),.Sum(Sum[1]),.Cout(C[1]));
FUAdder F3(.A(A[2]),.B(W[2]),.Cin(C[1]),.Sum(Sum[2]),.Cout(C[2]));
FUAdder F4(.A(A[3]),.B(W[3]),.Cin(C[2]),.Sum(Sum[3]),.Cout(Cout));
endmodule
```


## TESTBENCH:-

```
module Adder_Subtractor_tb();
    reg [3:0] A,B;
    reg Cin;
    wire [3:0] Sum;
    wire Cout;
    Adder_Subtractor uut(A,B,Cin,Sum,Cout);
    initial begin
        for(integer i=0;i<10;i=i+1) begin
            A=$random();
            B=$random();
            Cin=$random();
            #10;
            $display("A=%d,B=%d,Cin=%d,Sum=%d,Cout=%d",A,B,Cin,Sum,Cout);
            #10;
        end
    end
    initial begin
        #300;
        $finish();
    end
endmodule
```

## OUTPUT:-

```
A= 4,B= 1,Cin=1,Sum= 3,Cout=1
A= 3,B=13,Cin=1,Sum= 6,Cout=0
A= 5,B= 2,Cin=1,Sum= 3,Cout=1
A=13,B= 6,Cin=1,Sum= 7,Cout=1
A=13,B=12,Cin=1,Sum= 1,Cout=1
A= 6,B= 5,Cin=0,Sum=11,Cout=0
A= 5,B= 7,Cin=0,Sum=12,Cout=0
A=15,B= 2,Cin=0,Sum= 1,Cout=1
A= 8,B= 5,Cin=0,Sum=13,Cout=0
A=13,B=13,Cin=1,Sum= 0,Cout=1
```

## SCHEMATIC:-

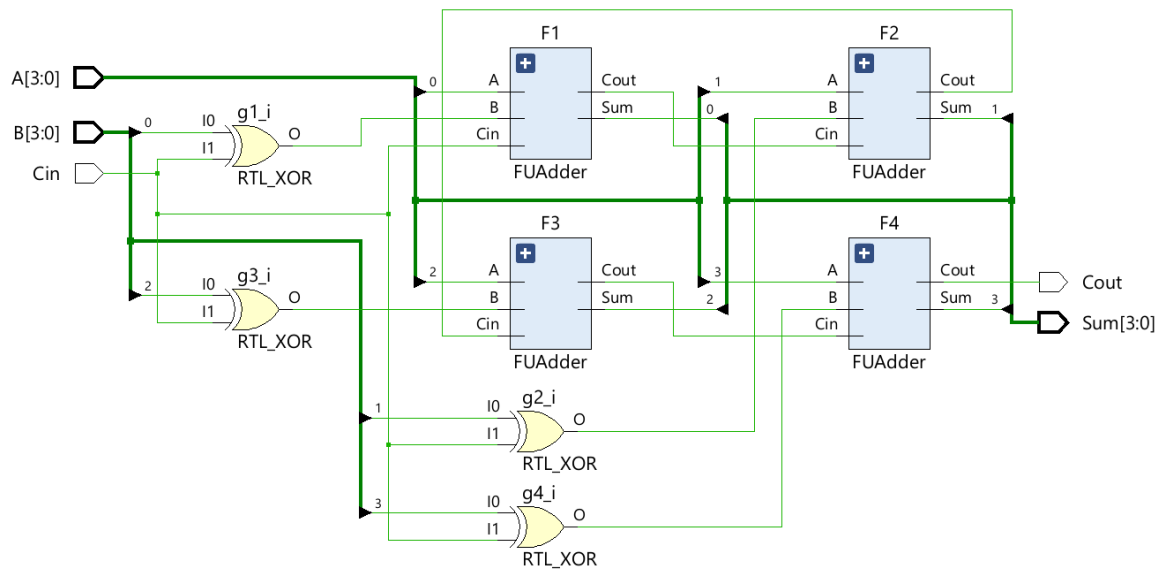

## WAVEFORMS:-

