



DAY-70

#100DAYSOFRTL


Aim:- Implementation of **T F/F TO SR F/F** using Verilog.

RTL CODE:-

```
///DATE:-10/03/2024
///DAY-70
///Implementation of T FF TO SR FF
module Day_70(input clk,rst,S,R,
output q,qbar);
wire w1,w2,w3;
and g1(w1,S,qbar);
and g2(w2,R,q);
or g3(w3,w1,w2);
Tff t1(clk,rst,w3,q,qbar);
endmodule

///T-Flipflop
module Tff(input clk,rst,T,
output reg q, output qbar);
always @(posedge clk) begin
if(rst) begin
q<=0;
end
else begin
case (T)
1'b0: {q}={q};
1'b1: {q}={~q};
endcase
end
end
assign qbar=~q;
endmodule
```

WAVEFORMS:-

 

TESTBENCH:-

```
module Day_70_tb();  
  reg clk,rst,S,R;  
  wire q,qbar;  
  Day_70 uut(clk,rst,S,R,q,qbar);  
  always #5 clk=~clk;  
  initial clk=0;  
  initial begin  
    rst=1; #10;  
    rst=0;  
    S=0; R=0; #20;  
    S=0; R=1; #30;  
    S=1; R=1; #20;  
    S=0; R=0; #30;  
    S=0; R=1; #30;  
    S=1; R=1; #20;  
  end  
  initial begin  
    #200;  
    $finish();  
  end  
end  
endmodule
```

SCHEMATIC:-

