 




DAY-81

#100DAYSOFRTL

Aim:- Implementation of Serial-in Serial-Out Shift Register Using JK Flip-Flop



RTL CODE:-


```
////DATE:-21/03/2024
////DAY-81
////////Implementation of Serial-in Serial Out using JK FF
module Day_81(input clk,rst,si, output so);
  wire [2:0] q;
  wire [3:0] qb;
  wire w1;
  not g1(w1,si);
  JKFF M1(clk,rst,si,w1,q[2],qb[3]);
  JKFF M2(clk,rst,q[2],qb[3],q[1],qb[2]);
  JKFF M3(clk,rst,q[1],qb[2],q[0],qb[1]);
  JKFF M4(clk,rst,q[0],qb[1],so,qb[0]);
endmodule

module JKFF(input clk,rst,J,K,
  output reg q, qbar);
  always@(posedge clk) begin
    if(rst) begin
      q<=0;
      qbar<=1;
    end
    else begin
      case({J,K})
        2'b00:{q,qbar}<={q,qbar};
        2'b01:{q,qbar}<={1'b0,1'b1};
        2'b10:{q,qbar}<={1'b1,1'b0};
        2'b11:{q,qbar}<={qbar,q};
      default: begin end
    endcase
  end
endmodule
```

TESTBENCH:-

```
module Day_81_tb();  
    reg clk,rst,si;  
    wire so;  
    Day_81 uut(clk,rst,si,so);  
    always #5 clk=~clk;  
    initial clk=0;  
    initial begin  
        rst=1; #10;  
        rst=0;  
        si=1; #10;  
        si=0; #10;  
        si=1; #10;  
        si=0; #10;  
        #50;  
        $finish();  
    end  
endmodule
```

WAVEFORMS:-

 

SCHEMATIC:-

