



DAY-7

#100DAYSOFRTL

Aim:- Implementation of Full Adder using Gate level Modelling.

RTL CODE:-

```
////DATE:-07/01/2024
////Full ADDER Using GatelevelModelling
module Fulladder(input A,B,C,
output Sum,Carry);
wire w1,w2,w3,w4;
xor g1(w1,A,B);
xor g2(Sum,w1,C);
and g3(w2,A,B);
and g4(w3,B,C);
and g5(w4,C,A);
or g6(Carry,w2,w3,w4);
endmodule
```

TESTBENCH:-

```
module Fulladder_tb();
reg A,B,C;
wire Sum,Carry;
Fulladder dut(A,B,C,
Sum,Carry);
initial begin
A=0;B=0;C=0;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=0;B=0;C=1;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=0;B=1;C=0;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=0;B=1;C=1;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=1;B=0;C=0;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=1;B=0;C=1;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=1;B=1;C=0;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
A=1;B=1;C=1;
#10;
$display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
end
```

```

○ $display("A=%b,B=%b,C=%b,Sum=%b,Carry=%b",A,B,C,Sum,Carry);
end
initial begin
○ #90;
○ → $finish;
end
endmodule

```


OUTPUT:-

```

A=0,B=0,C=0,Sum=0,Carry=0
A=0,B=0,C=1,Sum=1,Carry=0
A=0,B=1,C=0,Sum=1,Carry=0
A=0,B=1,C=1,Sum=0,Carry=1
A=1,B=0,C=0,Sum=1,Carry=0
A=1,B=0,C=1,Sum=0,Carry=1
A=1,B=1,C=0,Sum=0,Carry=1
A=1,B=1,C=1,Sum=1,Carry=1

```

SCHEMATIC:-

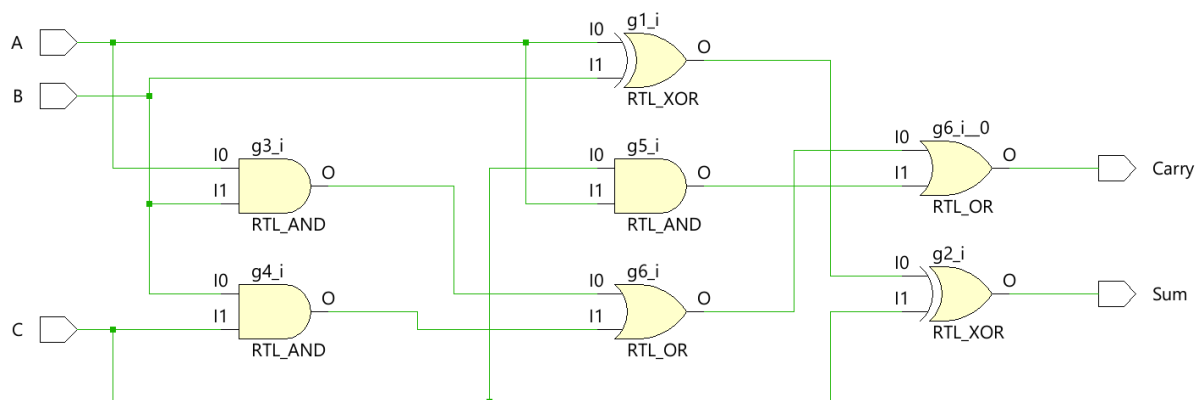

WAVEFORMS:-

